

I completed this assignment entirely on my own, except for discussions with Jiamin Xu.

Ethan Wong  
CSM51A

## Assignment 6

Input:  $n$  (5¢)    $d$  (10¢)    $g$  (gum)    $c$  (candy)

Output:  $N$  (5¢)    $D$  (10¢)    $G$  (gum)    $C$  (candy)

(This wasn't in the problem but I'll use 'D' as nothing gets outputted yet)

The different states for the machine should be based on how much money has been credited to the user

Change will be returned for values over 15 cents; all coins are multiples of 5.

### Possible States


$S_0$  : 0 cents credit  $\rightarrow$  0 coins

$S_1$  : 5 cents credit  $\rightarrow$  1 nickel

$S_2$  : 10 cents credit  $\rightarrow$  2 nickels, or 1 dime

$S_3$  : 15 cents credit  $\rightarrow$  3 nickels, or 1 dime + 1 nickel

### State Diagram

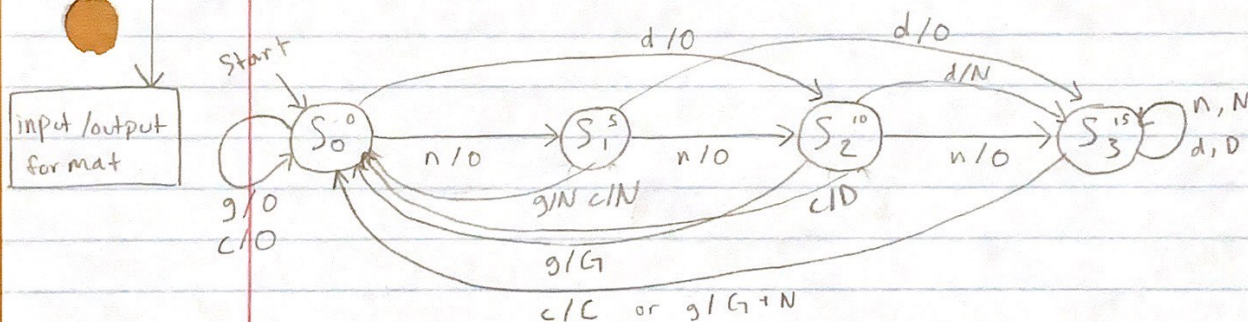

Flip Flops Needed : 2, because there are 4 total states



0¢      5¢      10¢      15¢  
AB      AB      AB      AB

State Table     $S_0: 00$      $S_1: 01$      $S_2: 11$      $S_3: 10$

N - Nickel input    d - Dime input    g - Request Gum    C - Request Candy

N - nickel output    D - dime output    G - Dispense Gum    C - Dispense Candy

Current State	Input	Next State	Flip Flops	Outputs
H A B	W Z	H A B	JA KA JB KB	N D G C
$S_0$ 0 0	0 0	$S_1$ 0 1	0 X 1 X	0 0 0 0
$S_0$ 0 0	0 1	$S_2$ 1 1	1 X 1 X	0 0 0 0
$S_0$ 0 0	1 1	$S_0$ 0 0	0 X 0 X	0 0 0 0
$S_0$ 0 0	1 0	$S_0$ 0 0	0 X 0 X	0 0 0 0
$S_1$ 0 1	0 0	$S_2$ 1 1	1 X X 0	0 0 0 0
$S_1$ 0 1	0 1	$S_3$ 1 0	1 X X 1	0 0 0 0
$S_1$ 0 1	1 1	$S_0$ 0 0	0 X X 1	1 0 0 0
$S_1$ 0 1	1 0	$S_0$ 0 0	0 X X 1	1 0 0 0
$S_2$ 1 1	0 0	$S_3$ 1 0	X 0 X 1	0 0 0 0
$S_2$ 1 1	0 1	$S_3$ 1 0	X 0 X 1	1 0 0 0
$S_2$ 1 1	1 1	$S_0$ 0 0	X 1 X 1	0 0 1 0
$S_2$ 1 1	1 0	$S_0$ 0 0	X 1 X 1	0 1 0 0
$S_3$ 1 0	0 0	$S_3$ 1 0	X 0 0 X	1 0 0 0
$S_3$ 1 0	0 1	$S_3$ 1 0	X 0 0 X	0 1 0 0
$S_3$ 1 0	1 1	$S_0$ 0 0	X 1 0 X	1 0 1 0
$S_3$ 1 0	1 0	$S_0$ 0 0	X 1 0 X	0 0 0 1

Because the inputs (inserting coins, requesting from machine) are mutually exclusive, I will assign values to WZ (the input variable)

WZ: 00 means a nickel was inserted

01 means a dime was inserted

11 means the user requested gum

10 means the user requested candy



Flip Flop JA

AB \ WZ	00	01	11	10
00	0	1	0	0
01	1	1	0	0
11	X	X	X	X
10	X	X	X	X

$$JA = (W' \cdot Z) + (B \cdot W')$$

KA

AB \ WZ	00	01	11	10
00	X	X	X	X
01	X	X	X	X
11	0	0	1	1
10	0	0	1	1

$$KA = W$$

JB

AB \ WZ	00	01	11	10
00	1	1	0	0
01	X	X	X	X
11	X	X	X	X
10	0	0	0	0

$$JB = A' \cdot W'$$

KB

AB \ WZ	00	01	11	10
00	X	X	X	X
01	0	1	1	1
11	1	1	1	1
10	X	X	X	X

$$KB = Z + W + A$$

Outputs N

AB \ WZ	00	01	11	10
00	0	0	0	0
01	0	0	1	1
11	0	1	0	0
10	1	0	1	0

$$N = (a' \cdot b \cdot w) + (a \cdot b' \cdot w' \cdot z') + (a \cdot b' \cdot w \cdot z) + (a \cdot b \cdot w' \cdot z)$$

D

AB \ WZ	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	0	1
10	0	1	0	0

$$D = (a \cdot b' \cdot w' \cdot z) + (a \cdot b \cdot w \cdot z')$$

G

AB \ WZ	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	1	0
10	0	0	1	0


$$G = a \cdot w \cdot z$$

C

AB \ WZ	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	0	0
10	0	0	0	1

$$C = a \cdot b' \cdot w \cdot z'$$



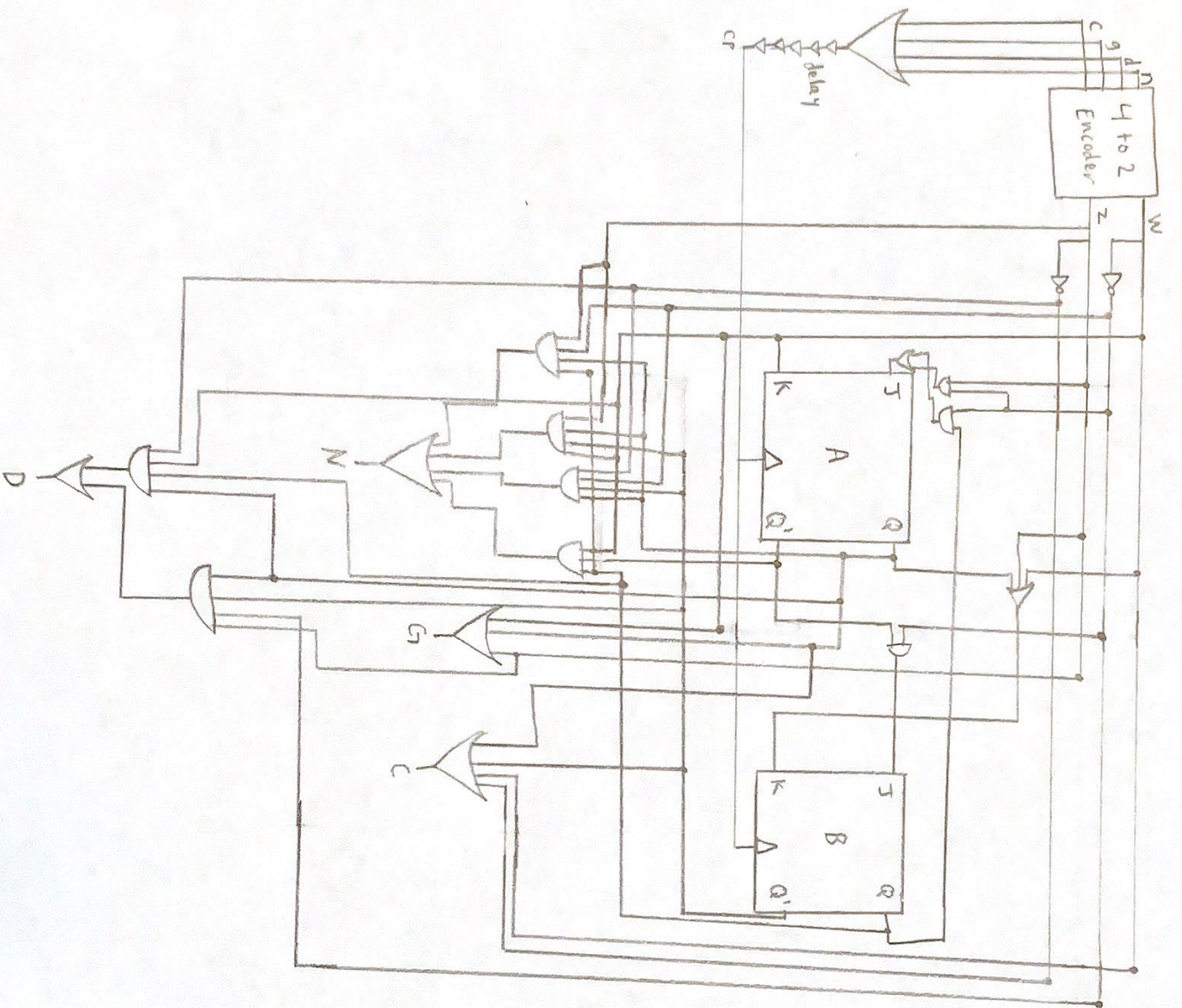

Sorry this is kind of messy, it was hard since some of the expressions were weird.